

DIGITAL LOGIC DESIGN

by

Dr. Fenghui Yao


**Tennessee State University
Department of Computer Science
Nashville, TN**

Definitions

◆ Switching network

- One or more inputs
- One or more outputs
- ✓ Two Types
 - Combinational
 - The output depends only on the present values of the inputs
 - Logic gates are used
 - Sequential
 - The output depends on present and past input values

Boolean Algebra

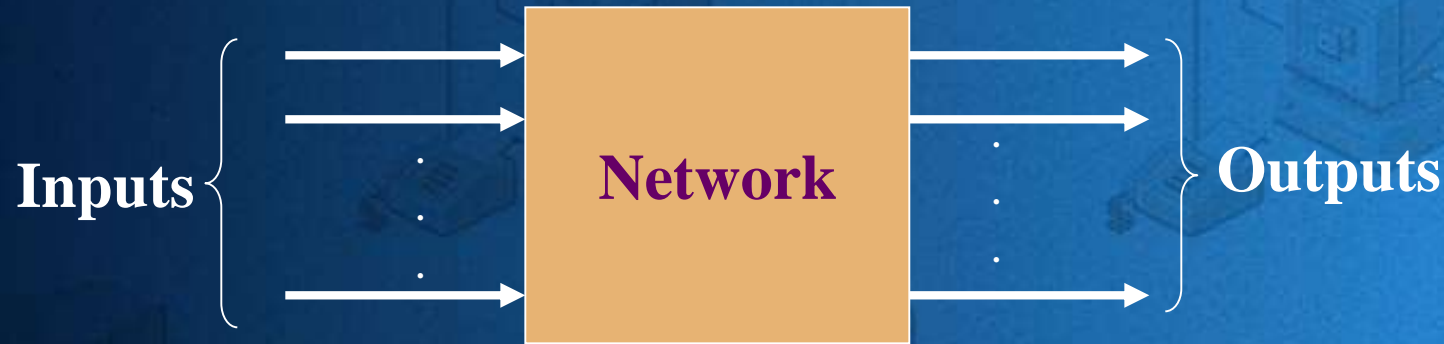

- ◆ **Boolean Algebra** is used to describe the relationship between inputs and outputs
- ◆ **Boolean Algebra** is the logic mathematics used for understanding of digital systems


Basic Operations

◆ COMPLEMENT (INVERSE)

$$0' = 1 \quad \text{and} \quad 1' = 0$$

$$A' = 1 \quad \text{if} \quad A = 0 \quad \text{and} \quad A' = 0 \quad \text{if} \quad A = 1$$

A	F
0	1
1	0

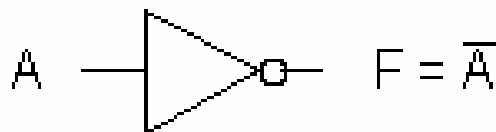


0 is low voltage

1 is high voltage

Basic Operations

◆ AND

A	B	F
0	0	0
0	1	0
1	0	0
1	1	1

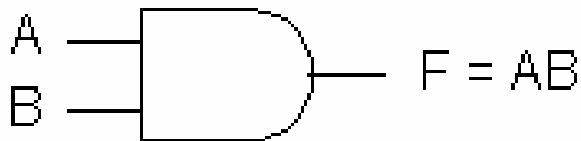


F is 1 if and only if

A and B are both 1

Basic Operations

◆ OR

A	B	F
0	0	0
0	1	1
1	0	1
1	1	1

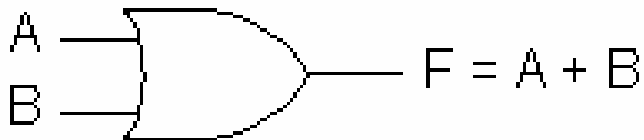

F is 1 if and only if

A or B (or both) are 1

Basic Theorems

$$X + 0 = X$$

$$X \cdot 1 = X$$

$$X + 1 = 1$$

$$X \cdot 0 = 0$$

$$X + X = X$$

$$X \cdot X = X$$

$$(X')' = X$$

$$X + XY = X$$

$$X + X' = 1$$

$$X(X + Y) = X$$

Let's prove each one

Simplification Theorems

$$1. \quad XY + XY' = X$$

$$2. \quad (X + Y)(X + Y') = X$$

$$3. \quad X + XY = X$$

$$4. \quad X(X + Y) = X$$

$$5. \quad (X + Y')Y = XY$$

$$6. \quad XY' + Y = X + Y$$

◆ **Proof 6.**

$$\text{R.H.S.} = X+Y$$

$$= X(Y+Y')+Y(X+X')$$

$$= XY+XY'+XY+X'Y$$

$$= XY+XY'+X'Y$$

$$= (X+X')Y+XY'$$

$$= Y+XY'$$

$$= \text{L.H.S.}$$

Truth Table

- ◆ It can represent a boolean function
- ◆ For possible input combinations it shows the output value
- ◆ There are 2^n rows (n is the number of input variables)
- ◆ It ranges from 0 to $2^n - 1$

Examples

- ◆ Show the truth table for

$$F = X' + YZ$$

- ◆ Show the followings by constructing truth tables


$$X(Y + Z) = XY + XZ$$

$$X + YZ = (X + Y)(X + Z)$$

Example

- ◆ Draw the network diagram for


$$F = X' + YZ$$

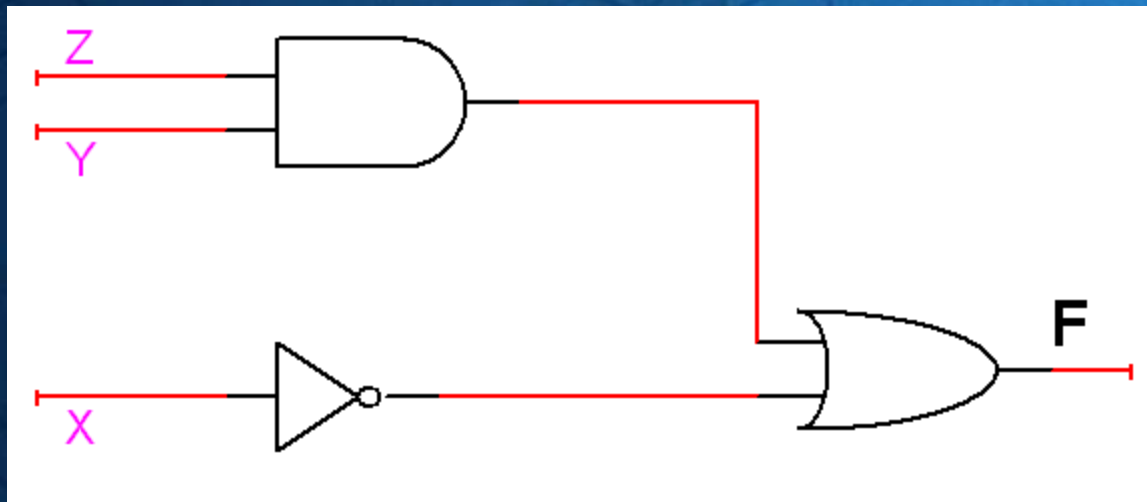

Example

- ◆ Draw the network diagram for

$$F = XYZ' + XY'Z + X'Y'$$

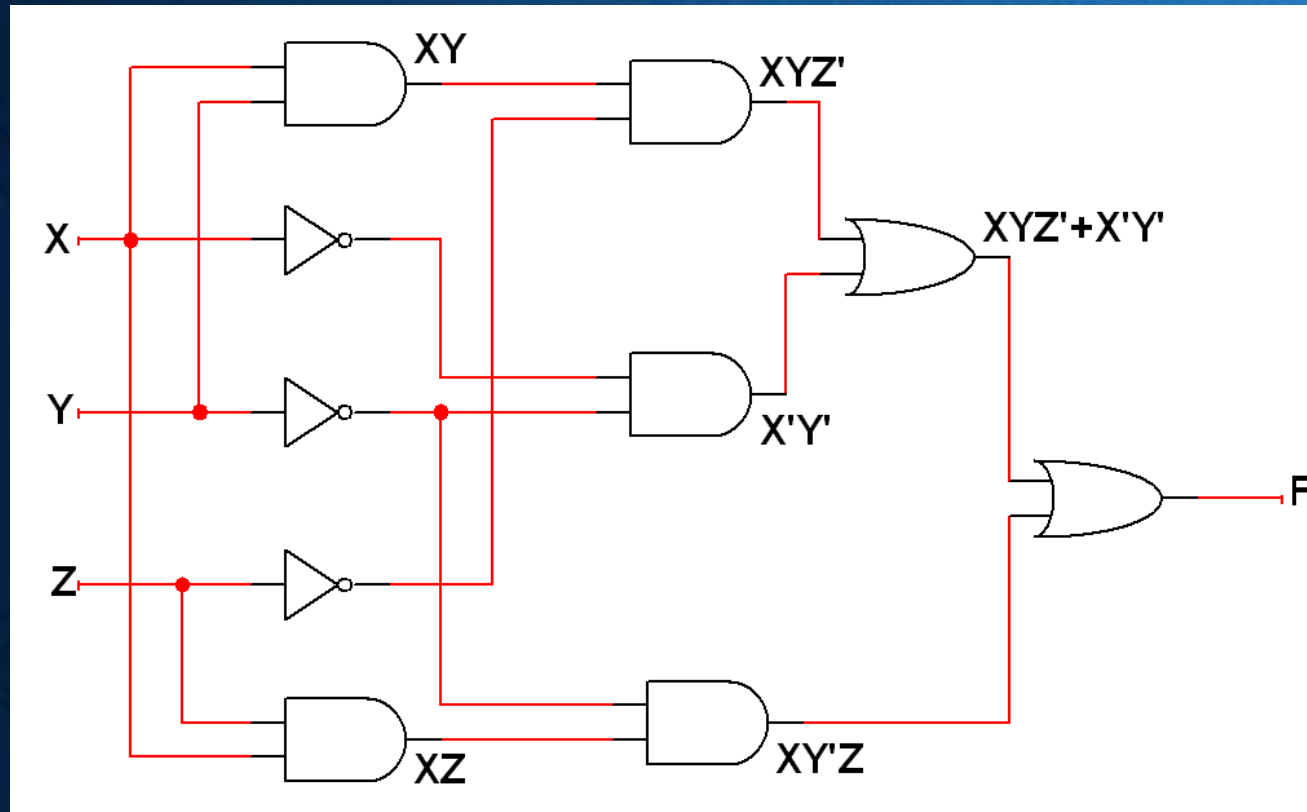

Operator Precedence

- ◆ Parenthesis
- ◆ NOT
- ◆ AND
- ◆ OR

Inversion

$$(X + Y)' = X'Y'$$

$$(XY)' = X' + Y'$$

Prove with the truth tables...

$$(X_1 + X_2 + \dots + X_n)' = X_1'X_2'\dots X_n'$$

$$(X_1X_2\dots X_n)' = X_1' + X_2' + \dots + X_n'$$

- ◆ The complement of the product is the sum of the complements
- ◆ The complement of the sum is the product of the complements

Examples

- ◆ Find the complements of

$$[(A' + B)C']' = ?$$

$$[(AB' + C)D' + E]' = ?$$

$$[A + ((BC')' + D)']'' = ?$$

Study Problems

1. Draw a network to realize the following by using only one AND gate and one OR gate

$$Y = ABCD + ABCE + ABCF$$

2. Draw a network to realize the following by using two OR gates and two AND gates

$$F = (V + W + X)(V + X + Y)(V + Z)$$

3. Prove the following equations using truth table

$$W'XY + WZ = (W' + Z)(W + XY)$$

$$(A + C)(AB + C') = AB + AC'$$

Solution of problem 2

$$\begin{aligned}\text{L.H.S.} &= (V+X+W)(V+X+Y)(V+Z) \\ &= [(V+X)+W(V+X)+Y(V+X)+WY](V+Z) \\ &= [(V+X)(1+W+Y)+WY](V+Z) \\ &= (V+X+WY)(V+Z)\end{aligned}$$

This can be implemented by two OR gates and two AND gate.

Minterms

- ◆ Consider variables A and B
- ◆ Assume that they are somehow combined with AND operator
- ◆ There are 4 possible combinations

$$AB, A'B, AB', A'B'$$

- ◆ Each of those terms is called a minterm (standard product)
- ◆ In general, if there are n variables, there are 2^n minterms

Exercise

- ◆ List the minterms for 3 variables

A	B	C	Minterm	Designation
0	0	0	$A' B' C'$	m_0
0	0	1	$A' B' C$	m_1
0	1	0	$A' B C'$	m_2
0	1	1	$A' B C$	m_3
1	0	0	$A B' C'$	m_4
1	0	1	$A B' C$	m_5
1	1	0	$A B C'$	m_6
1	1	1	$A B C$	m_7

Maxterms

- ◆ Consider variables A and B
- ◆ Assume that they are somehow combined with OR operator
- ◆ There are 4 possible combinations

$$A + B, \quad A' + B, \quad A + B', \quad A' + B'$$

- ◆ Each of those terms is called a maxterm (standard sums)
- ◆ In general, if there are n variables, there are 2^n maxterms

Exercise

- ◆ List the maxterm for 3 variables

A	B	C	Maxterm	Designation
0	0	0	$A+B+C$	M_0
0	0	1	$A+B+C'$	M_1
0	1	0	$A+B'+C$	M_2
0	1	1	$A+B'+C'$	M_3
1	0	0	$A'+B+C$	M_4
1	0	1	$A'+B+C'$	M_5
1	1	0	$A'+B'+C$	M_6
1	1	1	$A'+B'+C'$	M_7

Example

- ◆ Express F in the sum of minterms and product of maxterms formats

$$F = A + BC'$$

$$\begin{aligned} F &= A + BC' = A(B + B')(C + C') + (A + A')BC' \\ &= ABC + ABC' + AB'C + AB'C' + ABC' + A'BC' \\ &= ABC + ABC' + AB'C + AB'C' + A'BC' \\ &= m_7 + m_6 + m_5 + m_4 + m_2 \\ &= \sum(2,4,5,6,7) \\ &= \prod(0,1,3) \end{aligned}$$

Sum-of-Products

- ◆ All products are the product of single variable only

$$AB' + CD'E + AC'E' \leftarrow \text{YES}$$


$$A + B' + C + D'E \leftarrow \text{YES}$$

$$(A + B)CD + EF \leftarrow \text{NO}$$

Sum-of-Products

- ◆ One or more AND gates feeding a single OR gate at the output

$$AB' + CD'E + AC'E'$$

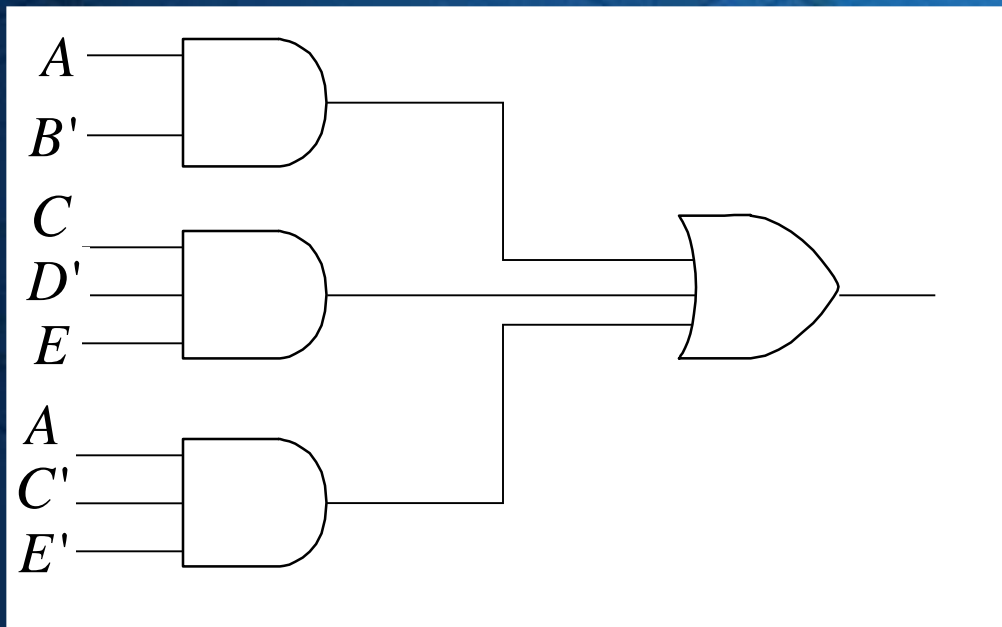

Product-of-Sums

- ◆ All sums are the sums of single variables

$$(A + B')(C + D' + E)(A + C' + E') \leftarrow \text{YES}$$


$$AB'C(D' + E) \leftarrow \text{YES}$$

$$(A + B)(C + D) + EF \leftarrow \text{NO}$$

Product-of-Sums

- ◆ One or more OR gates feeding a single AND gate at the output


$$(A + B')(C + D' + E)(A + C' + E')$$

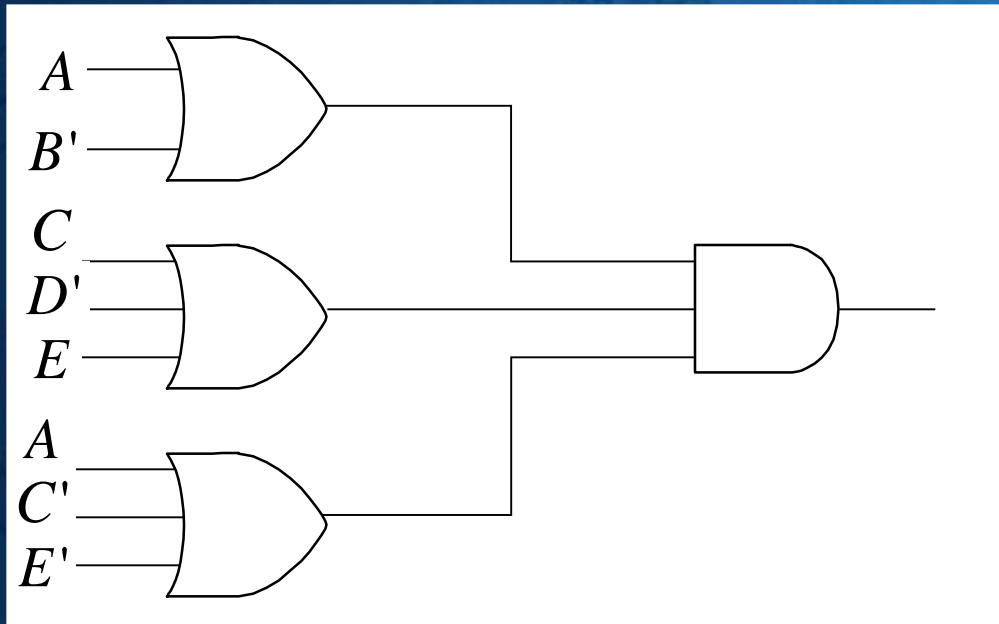

Logic Gates


$$F = A \uparrow B$$

A	B	F
0	0	1
0	1	1
1	0	1
1	1	0

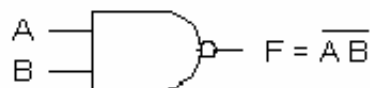

NAND


A	B	F
0	0	1
0	1	0
1	0	0
1	1	0

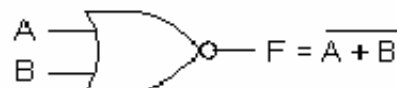

NOR


$$F = A \downarrow B$$

A	B	F
0	0	0
0	1	1
1	0	1
1	1	0

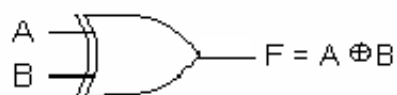

Exclusive-OR (XOR)


A	B	F
0	0	1
0	1	0
1	0	0
1	1	1

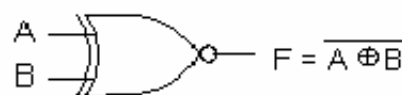

Exclusive-NOR (XNOR)

Exclusive-OR

A	B	F
0	0	0
0	1	1
1	0	1
1	1	0

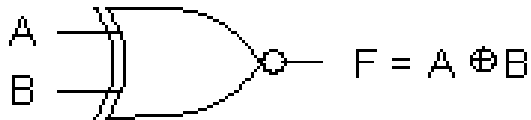

Exclusive-OR (XOR)

$$A \oplus 0 = A$$

$$A \oplus 1 = A'$$

$$A \oplus A = 0$$

$$A \oplus A' = 1$$

$$A \oplus B = B \oplus A$$

$$(A \oplus B) \oplus C = A \oplus (B \oplus C) = A \oplus B \oplus C$$

$$A(B \oplus C) = AB \oplus AC$$


$$(A \oplus B)' = A \oplus B' = A' \oplus B = AB + A'B'$$

$$A \oplus B = 1 \Leftrightarrow A = 1 \text{ or } B = 1 \text{ but not both}$$

Equivalence

- ◆ Equivalence is the complement of exclusive-OR
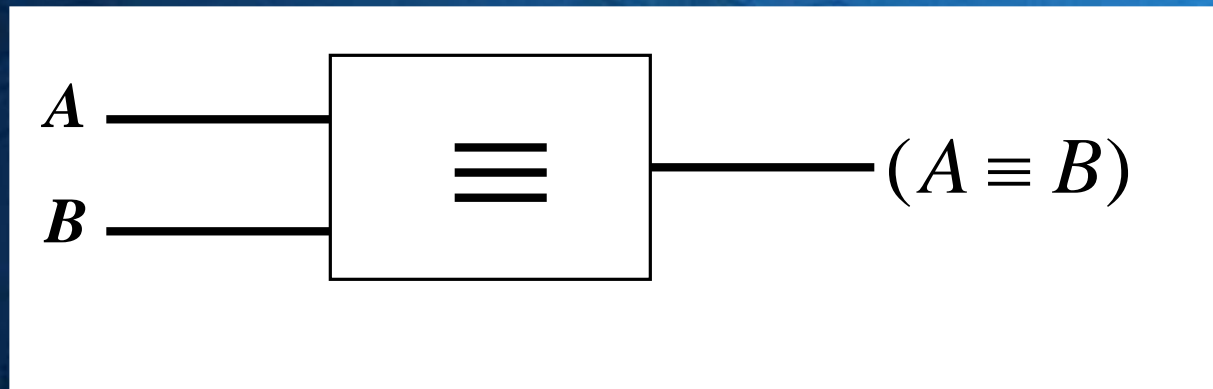
$$(A \oplus B)' = (A'B + AB')' = (A + B')(A' + B) = AB + A'B' = (A \equiv B)$$



$$F = (A'B \equiv C) + (B \oplus AC')$$

Simplify it...

Integrated Circuits

- ◆ **SSI (Small Scale)**
 - **Less than 10 gates in a package**
- ◆ **MSI (Medium Scale)**
 - **10-1000 gates in a package**
- ◆ **LSI (Large Scale)**
 - **1000s of gates in a single package**
- ◆ **VLSI (Very Large Scale)**
 - **Hundred of thousands of gates in a single package**

Study Problems

◆ Course Book Chapter – 2 Problems

- 2 – 1
- 2 – 3
- 2 – 5
- 2 – 8
- 2 – 12
- 2 – 14

Questions

