

Digital Electronics

Principles & Applications

Fifth Edition


Roger L. Tokheim

Chapter 10

Arithmetic Circuits

©1999

Glencoe/McGraw-Hill

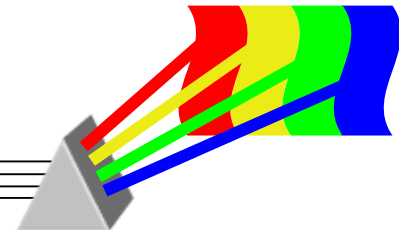

CHAPTER 10 PREVIEW

- **Binary Addition**
- **Half & Full Adders**
- **Binary Subtraction**
- **Half & Full Subtractors**
- **Parallel Adders and Subtractors**
- **Using Adders for Subtraction**
- **Binary Multiplication**
- **Binary Multipliers**
- **Half & Full Adders**
- **2s Complement**

BINARY ADDITION

- Conceptually similar to decimal addition
- *Example:* Add the binary numbers 1010 and 11

A binary addition diagram showing the sum of 1010 and 11. The numbers are aligned by their least significant bits. A horizontal green line separates the addends from the result. The result is 1101. A red curved arrow labeled '(carry) 1' points from the third column (from the right) to the fourth column, indicating a carry-out.

$$\begin{array}{r} \text{(carry)} \\ 1 \\ 1010 \\ + \quad 11 \\ \hline 1101 \end{array}$$



TEST


Add the Binary numbers 11010 and 1100

$$\begin{array}{r} \text{(carry)} \text{(carry)} \\ \begin{array}{r} 1 \quad 1 \\ 1 \quad 1 \quad 0 \quad 1 \quad 0 \\ + \quad 1 \quad 1 \quad 0 \quad 0 \\ \hline 1 \quad 0 \quad 0 \quad 1 \quad 1 \quad 0 \end{array} \end{array}$$


HALF ADDER

- Logic device that adds two binary numbers
- Only adds Least Significant Digit (LSD) column (1s column) in binary addition

Logic
Symbol:

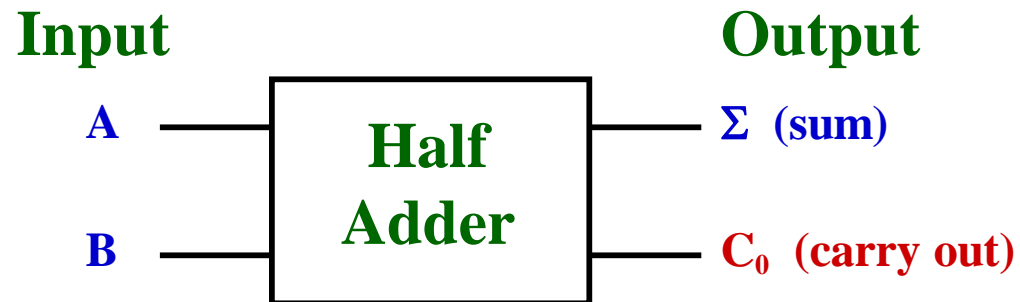


Logic
Diagram:

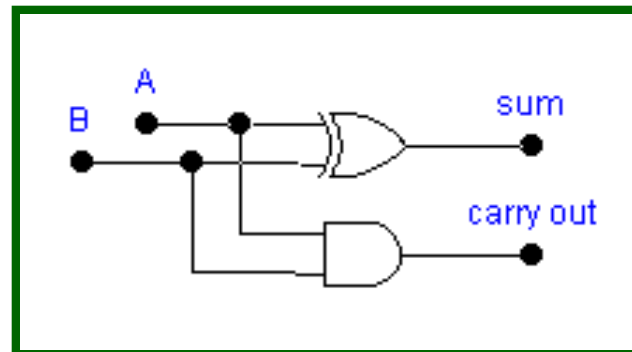


FULL ADDER

Used for adding binary place values other than the 1s place

Logic Symbol:

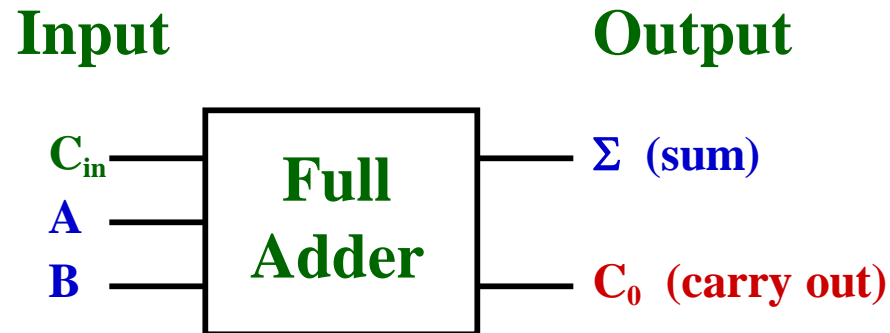

Logic Diagram:

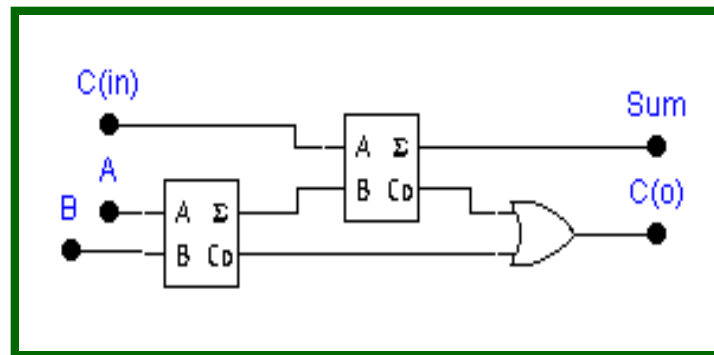

BINARY SUBTRACTION

Example: Subtract binary number 101 from 1011

(borrow)

$$\begin{array}{r} \\ \\ \\ - \\ \hline \end{array}$$

0 1 0 1 1
1 0 1 1
- 1 0 1
0 1 1 0



TEST


Subtract binary number 11 from 1010

$$\begin{array}{r} 01 \\ 0 \cancel{10} 0 \\ \cancel{1} \cancel{0} \cancel{1} 0 \\ - 1 \\ \hline 0 1 1 \end{array}$$


HALF SUBTRACTOR

Subtracts LSD column in binary subtraction

Logic
Symbol:

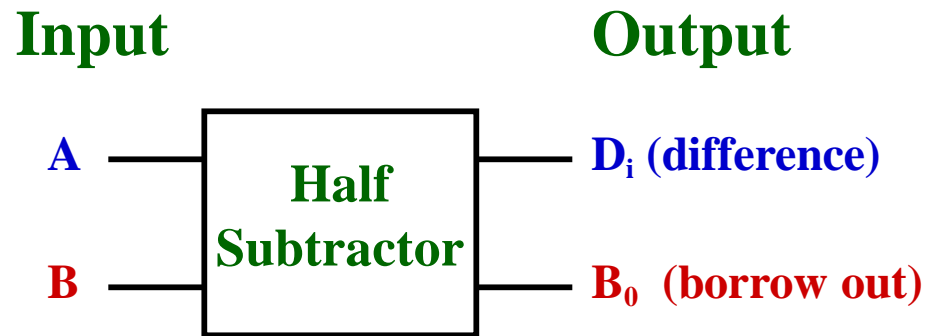


Logic
Diagram:

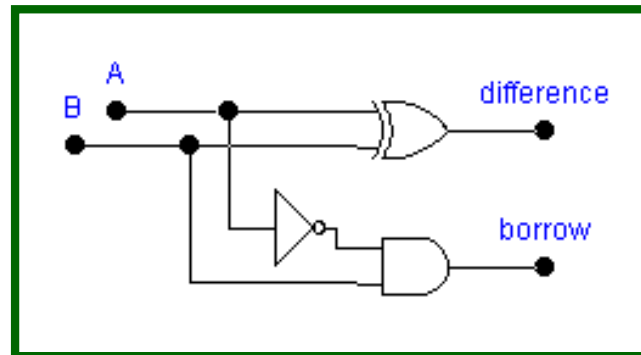


FULL SUBTRACTOR

Used for subtracting binary place values other than the 1s place

Logic
Symbol:

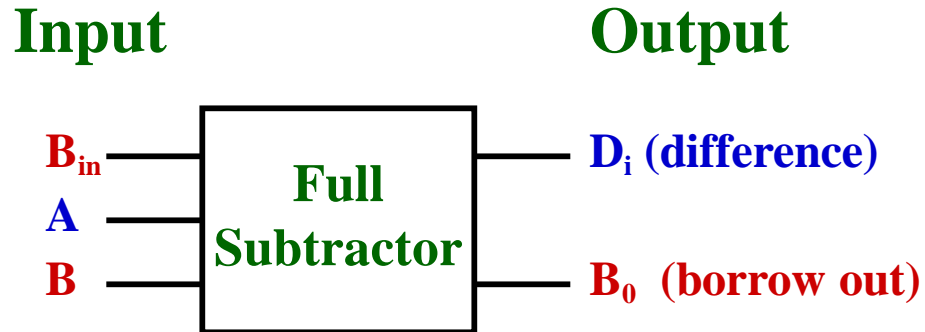


Logic
Diagram:

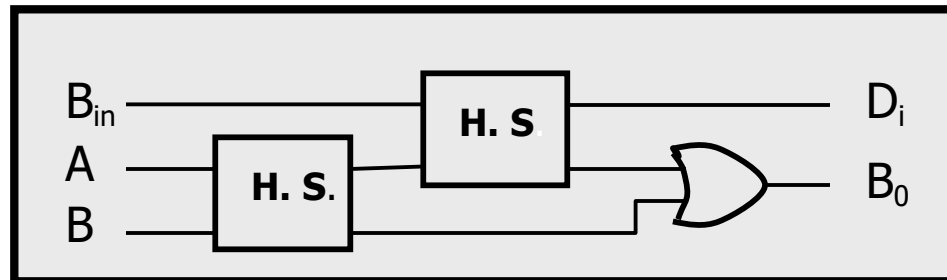

PARALLEL ADDING

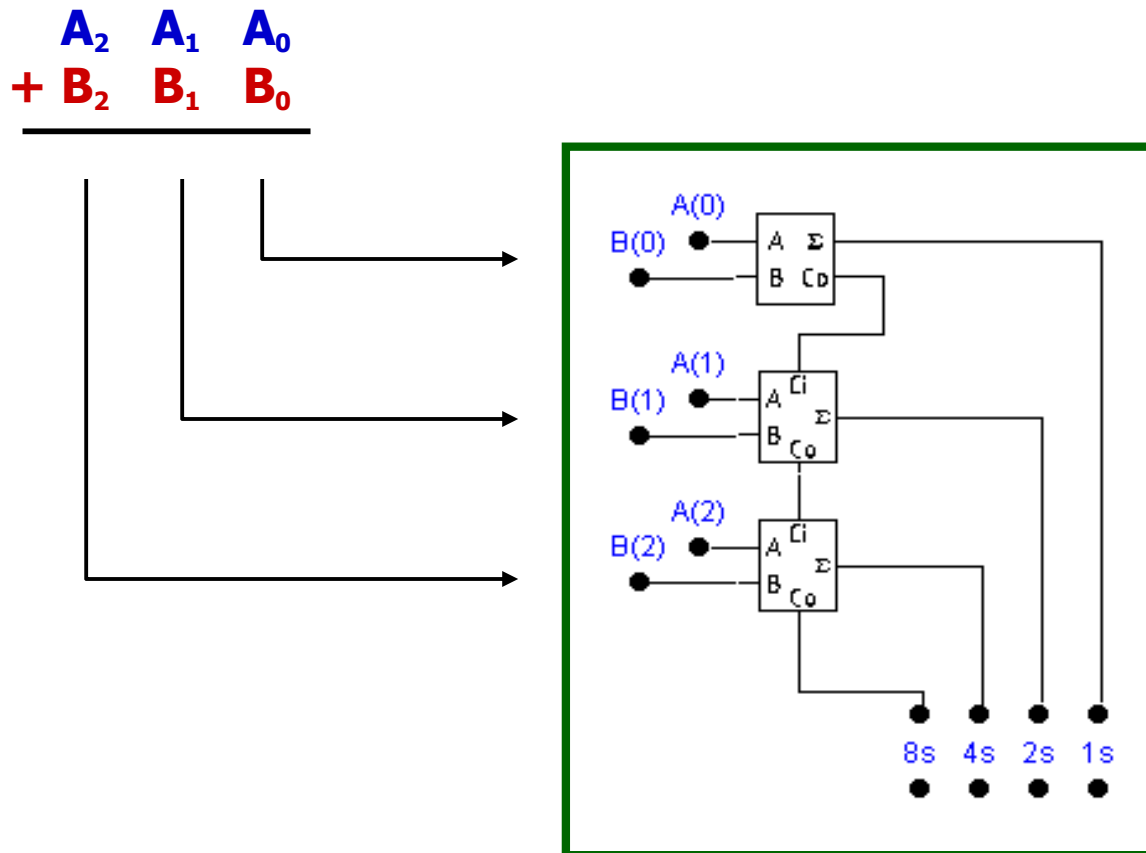
- Use half adder for LSD
- Use full adder for other digits



PARALLEL ADDER

Enter binary numbers
to be added

1 1 1 0 + 0 1 1 0

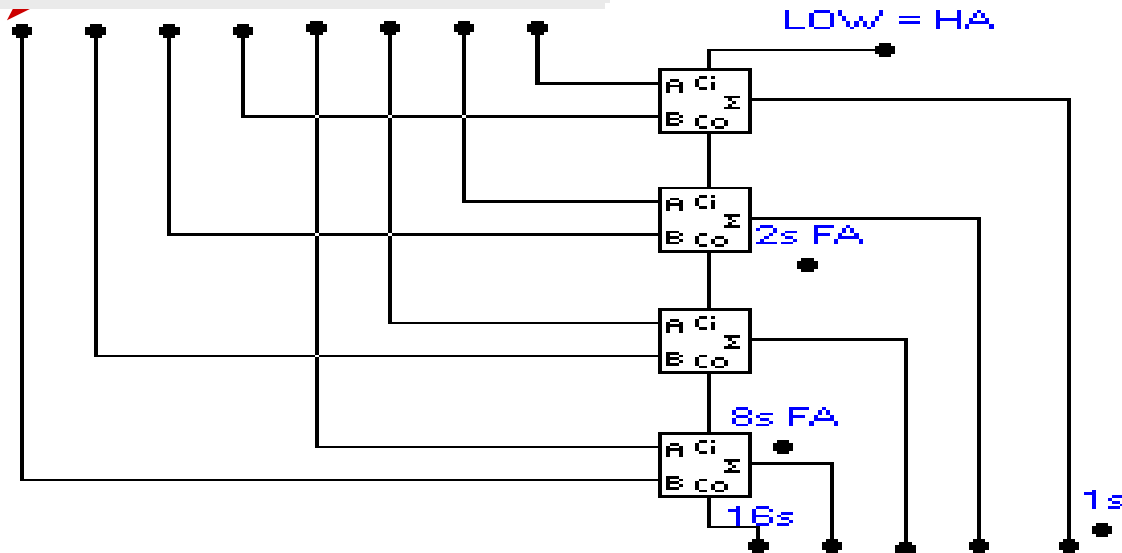

1 0 1 0 0

Parallel adders are available in IC form.

1s place uses half-adder

2s, 4s, 8s places use full adders

PARALLEL SUBTRACTOR USING FULL ADDERS


Binary numbers to
subtracted are input

1 0 0 1 - 0 1 1 1

HIGH at Carry in input acts like
adding +1 to a 1s C number to
form the 2s complement.
1sC is formed by four inverters.

HIGH = 1

Inverters

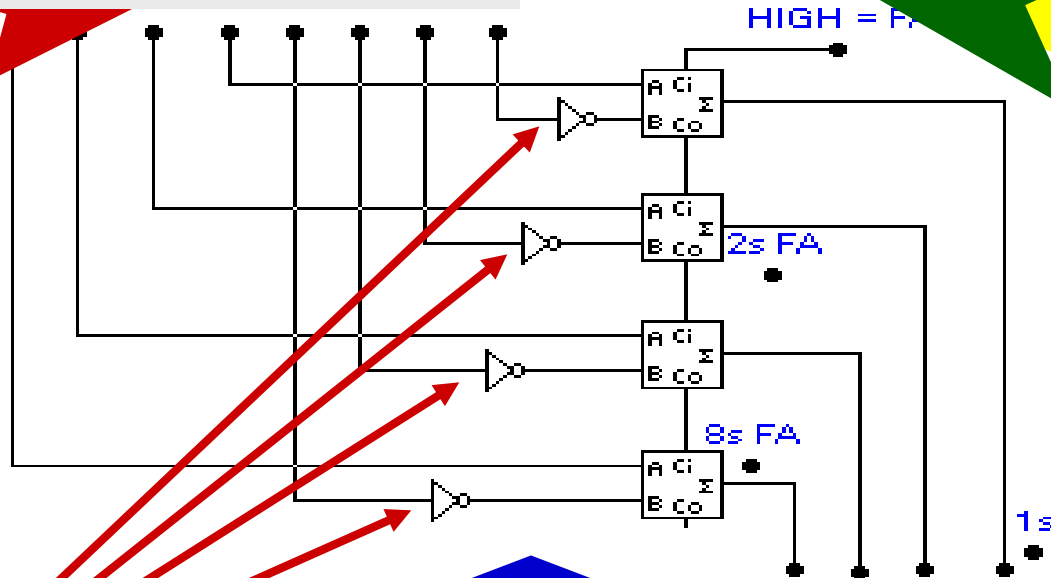

0 0 1 0

Note the use

The result (difference) of the
subtraction problem will appear here.

Also notice the addition of four
inverters on the B inputs to the FAs

BINARY MULTIPLICATION

Example: Multiply the binary numbers 111 and 101.

			1	1	1	Multiplicand
		x	1	0	1	Multiplier
<hr/>						
			1	1	1	1st partial product
		0	0	0		2nd partial product
	1	1	1			3rd partial product
<hr/>						
1	0	0	0	1	1	Product


111 x 101 can also be calculated: 111 + 111 + 111 + 111 + 111


$$\begin{array}{r}
 101 \\
 \times 100 \\
 \hline
 000 \\
 000 \\
 101 \\
 \hline
 10100
 \end{array}$$

BINARY MULTIPLIERS


Binary multiplier circuits - utilize repeated addition.

**Block
Diagram:**

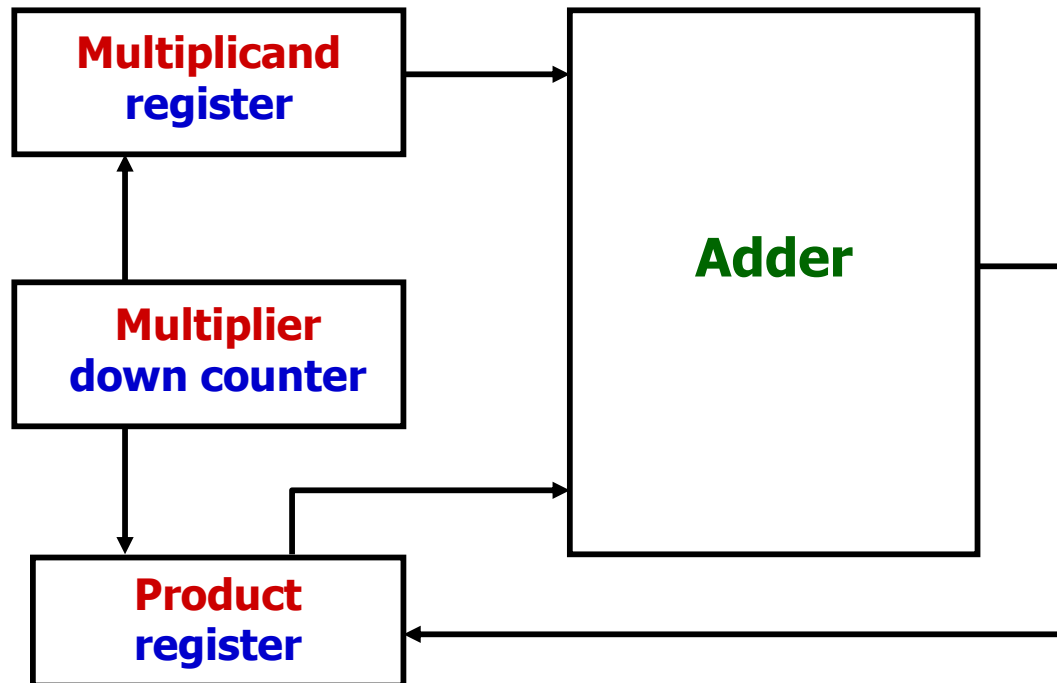

2s COMPLEMENT NOTATION

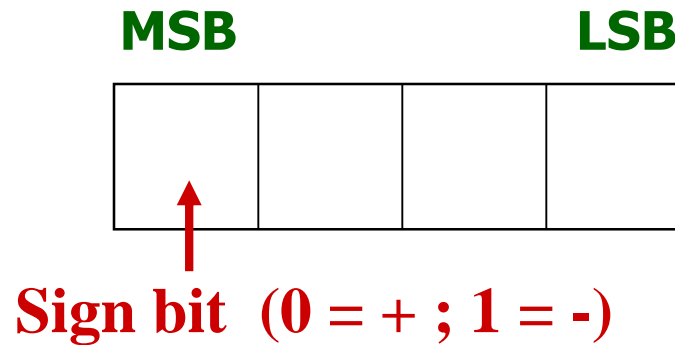- 2s complement representation - widely used in microprocessors.
- Represents *sign* and *magnitude*



Decimal:	+7	+4	+1	0	-1	-4	-7
2s Complement:	0111	0100	0001	0000	1111	1100	1001

2s COMPLEMENT - CONVERSIONS

- **Converting positive numbers to 2s complement:**
 - Same as converting to binary
- **Converting negative numbers to 2s complement:**

Decimal to 2s Complement

- 4 (decimal)

0 1 0 0

1 0 1 1

- 4 = 1 1 0 0 (2s Complement)

Convert decimal
to binary

1s
complement

Add 1

2s Complement to Binary

1 1 0 0 (2s C)

0 0 1 1

0 1 0 0 (Binary)

1s
complement

Add 1

ADDING/SUBTRACTING IN 2s COMPLEMENT

2s complement notation makes it possible
to add and subtract signed numbers

(Decimal)

$$\begin{array}{r} (-1) \\ + (-2) \\ \hline (-3) \end{array}$$

2s

Complement

$$\begin{array}{r} 1111 \\ + 1110 \\ \hline \end{array}$$

$$\begin{array}{r} 11101 \end{array}$$

2s complement

Discard

$$\begin{array}{r} (+1) \\ + (-3) \\ \hline (-2) \end{array}$$

$$\begin{array}{r} 0001 \\ + 1101 \\ \hline 1110 \end{array}$$

2s complement



TEST

Add the following 2s complement numbers:

$$\begin{array}{r} (+5) \\ + (-4) \\ \hline (+1) \end{array} \quad \begin{array}{r} 0101 \\ + 1100 \\ \hline 10001 \end{array}$$

Discard

PRACTICAL SUGGESTION FOR BINARY MATH

- **Use a scientific calculator.**
- **Most scientific calculators have DEC, BIN, OCT, and HEX modes and can either convert between codes or perform arithmetic in different number systems.**
- **Most scientific calculators also have other functions that are valuable in digital electronics such as AND, OR, NOT, XOR, and XNOR logic functions.**

